

# Computer Organization and Architecture

## Module 4-a

### Data Path and Control Path Example with Verilog

**Prof. Indranil Sengupta**

**Dr. Sarani Bhattacharya**

**Department of Computer Science and Engineering**

**IIT Kharagpur**


# **Data Path and Control Path**


# Introduction


- In a complex digital system, the hardware is typically partitioned into two parts:
  - a) Data Path*, which consists of the functional units where all computations are carried out.
    - Typically consists of registers, multiplexers, bus, adders, multipliers, counters, and other functional blocks.
  - b) Control Path*, which implements a finite-state machine and provides control signals to the data path in proper sequence.
    - In response to the control signals, various operations are carried out by the data path.
    - Also takes inputs from the data path regarding various status information.
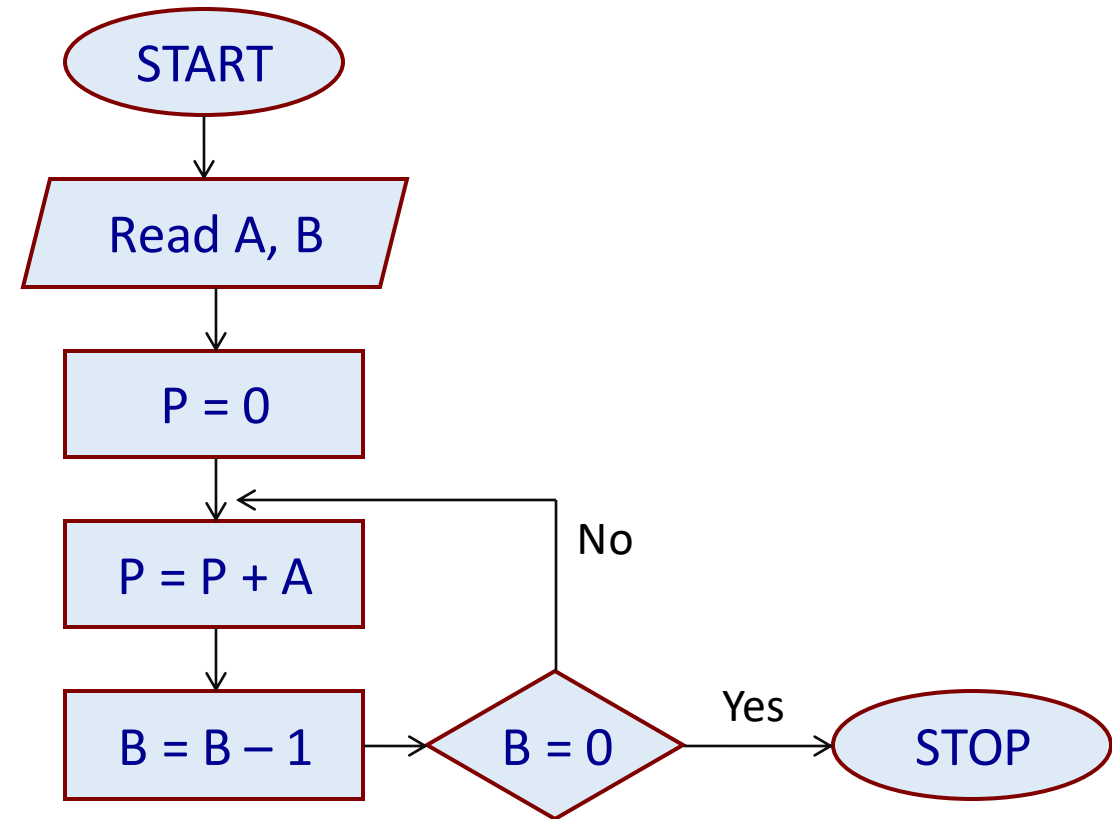
# Example 1: Multiplication by Repeated Addition


- We consider a simple algorithm using repeated addition.
  - Assume B is non-zero.
- We identify the functional blocks required in the data path, and the corresponding control signals.
- Then we design the FSM to implement the multiplication algorithm using the data path.



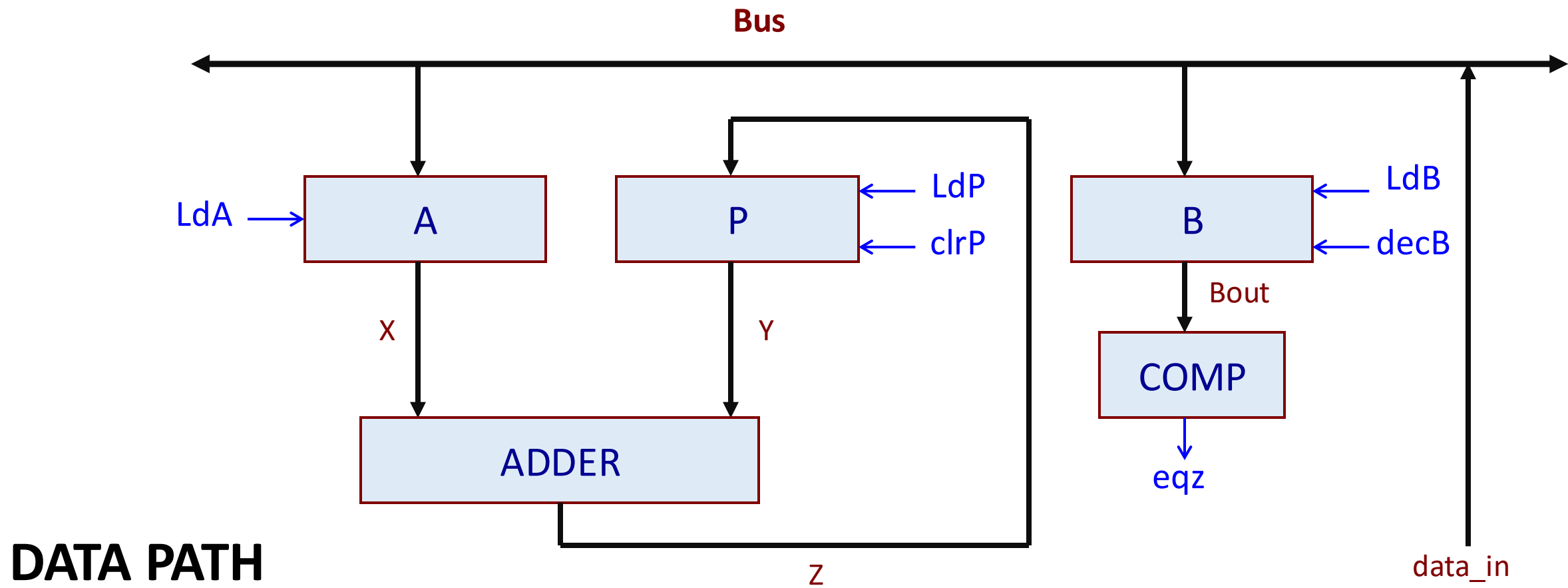


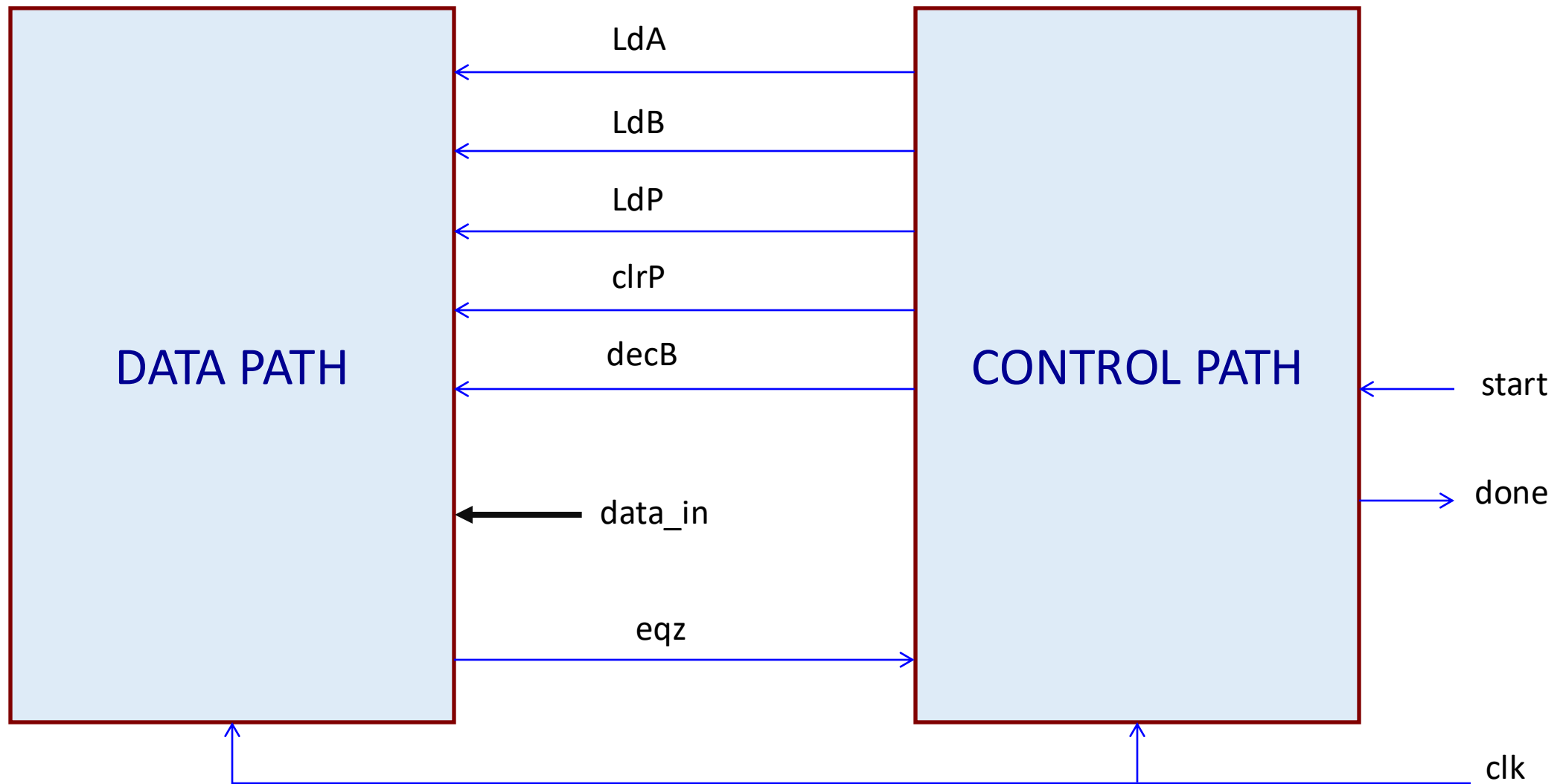


# CONTROL PATH

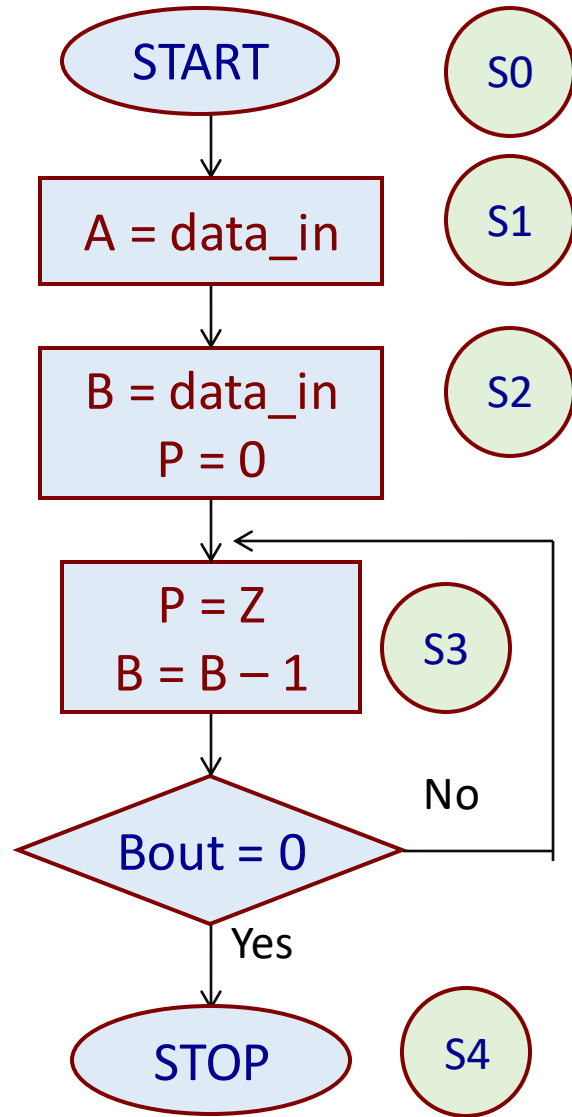

Micro-operations

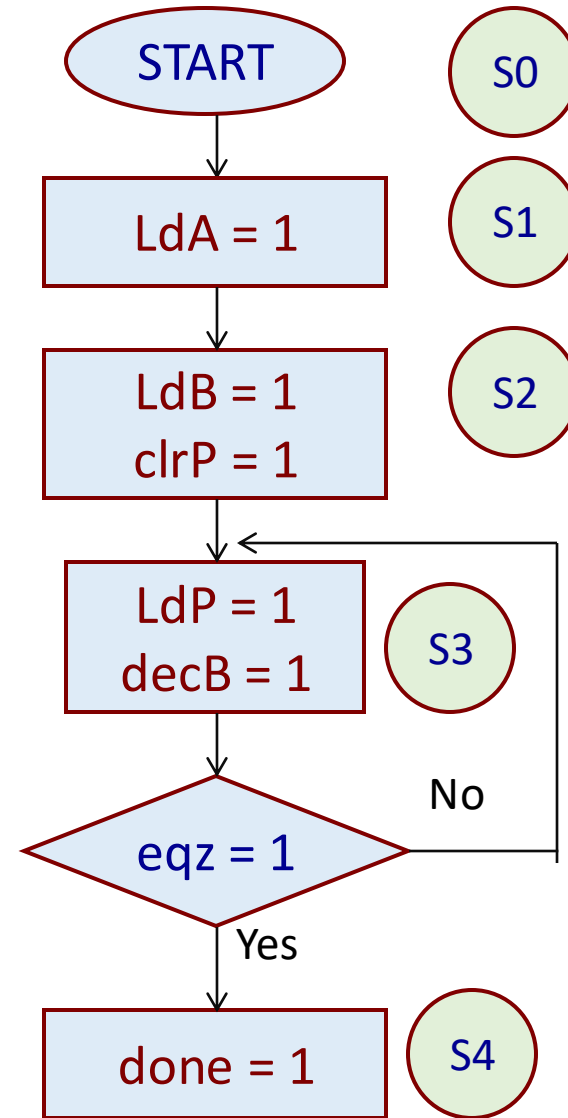

Control Signals

 

State Transitions

```
module MUL_datapath (eqz, LdA, LdB, LdP, clrP, decB, data_in, clk);  
    input LdA, LdB, LdP, clrP, decB, clk;  
    input [15:0] data_in;  
    output eqz;  
    wire [15:0] X, Y, Z, Bout, Bus;  
  
    PIP01 A (X, Bus, LdA, clk);  
    PIP02 P (Y, Z, LdP, clrP, clk);  
    CNTR B (Bout, Bus, LdB, decB, clk);  
    ADD AD (Z, X, Y);  
    EQZ COMP (eqz, Bout);  
endmodule
```

## THE DATA PATH



```

module PIP01 (dout, din, ld, clk);
    input [15:0] din;
    input ld, clk;
    output reg [15:0] dout;

    always @(posedge clk)
        if (ld) dout <= din;
endmodule

```

```

module ADD (out, in1, in2);
    input [15:0] in1, in2;
    output reg [15:0] out;

    always @(*)
        out = in1 + in2;
endmodule

```

```

module PIP02 (dout, din, ld,
              clr, clk);

    input [15:0] din;
    input ld, clr, clk;
    output reg [15:0] dout;

    always @(posedge clk)
        if (clr) dout <= 16'b0;
        else if (ld) dout <= din;
endmodule

```

```

module EQZ (eqz, data);
    input [15:0] data;
    output eqz;

    assign eqz = (data == 0);
endmodule

```

```
module CNTR (dout, din, ld, dec, clk);  
    input [15:0] din;  
    input ld, dec, clk;  
    output reg [15:0] dout;  
  
    always @(posedge clk)  
        if (ld) dout <= din;  
        else if (dec) dout <= dout - 1;  
endmodule
```

```
module controller (LdA, LdB, LdP, clrP, decB, done, clk, eqz, start);  
    input clk, eqz, start;  
    output reg LdA, LdB, LdP, clrP, decB, done;  
  
    reg [2:0] state;  
    parameter S0=3'b000, S1=3'b001, S2=3'b010, S3=3'b011, S4=3'b100;  
  
    always @(posedge clk)  
        begin  
            case (state)  
                S0:    if (start) state <= S1;  
                S1:    state <= S2;  
                S2:    state <= S3;  
                S3:    #2 if (eqz) state <= S4;  
                S4:    state <= S4;  
                default: state <= S0;  
            endcase  
        end  
end
```

**THE CONTROL  
PATH**

```
always @(state)
begin
    case (state)
        S0:    begin #1 LdA = 0;  LdB = 0; LdP = 0; clrP = 0; decB = 0; end
        S1:    begin #1 LdA = 1; end
        S2:    begin #1 LdA = 0; LdB = 1; clrP = 1; end
        S3:    begin #1 LdB = 0; LdP = 1; clrP = 0; decB = 1; end
        S4:    begin #1 done = 1; LdB = 0; LdP = 0; decB = 0; end
        default: begin #1 LdA = 0; LdB = 0; LdP = 0; clrP = 0; decB = 0; end
    endcase
end
endmodule
```

## THE TEST BENCH

0	x	x
6	x	0
35	0	0
45	17	0
55	34	0
65	51	0
75	68	0
85	85	0
88	85	1

```
module MUL_test;  
  reg [15:0] data_in;  
  reg clk, start;  
  wire done;
```

```
MUL_datapath DP (eqz, LdA, LdB, LdP, clrP, decB, data_in, clk);  
controller CON (LdA, LdB, LdP, clrP, decB, done, clk, eqz, start);
```

```
initial  
  begin  
    clk = 1'b0;  
    #3 start = 1'b1;  
    #500 $finish;  
  end  
  
always #5 clk = ~clk;
```

```
  initial  
    begin  
      #17 data_in = 17;  
      #10 data_in = 5;  
    end  
  initial  
    begin  
      $monitor ($time, " %d %b", DP.Y, done);  
      $dumpfile ("mul.vcd"); $dumpvars (0, MUL_test);  
    end  
  
endmodule
```